

2020

(Held in 2021)

PHYSICS

(Major)

Paper : 5.4

(**Electronics**)

Full Marks : 42

Time : 2 hours

*The figures in the margin indicate full marks
for the questions*

GROUP—A

(Marks : 21)

1. Answer the following questions briefly : $1 \times 2 = 2$

(a) Write the full form of CMRR.

(b) Name the type of feedback necessary to increase stability and bandwidth of an amplifier.

(2)


2. Write short answer to the following questions : 2×2=4

(a) State the reasons for which voltage gain of RC-coupled transistor amplifier continuously decreases in the high frequency range.

(b) State Barkhausen's criterion for sustained oscillation.

3. Answer any *three* of the following questions : 5×3=15

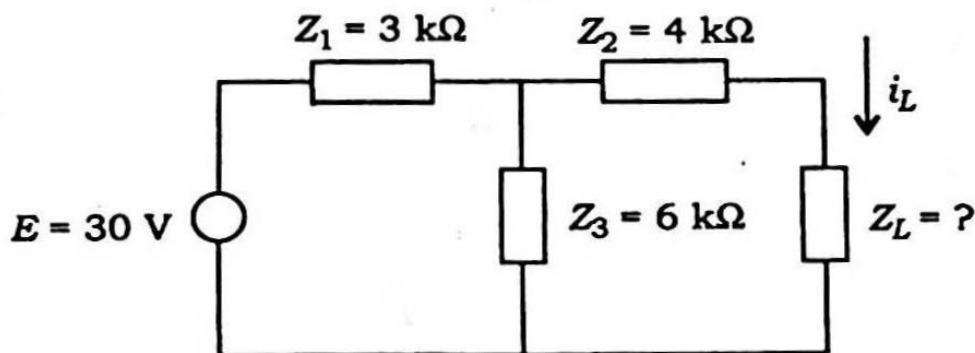(a) Convert the following circuit into Thevenin's equivalent circuit and find the Thevenin's equivalent impedance and voltage. Find the value of load impedance Z_L when load current (i_L) is 2 mA : 2+2+1=5



- (b) Draw the circuit diagram of a half-wave diode rectifier. Derive the expressions for d.c. for average and RMS value of current from the output waveform and hence find its efficiency. $1+1+1+2=5$
- (c) Convert the decimal numbers 37.75_{10} and 15.25_{10} into its binary equivalent and find the binary sum. Also find difference of these binary numbers by converting the smaller number into negative number. $3+2=5$
- (d) What are the variables related to input and output of a transistor when it is considered as a two-port four-terminal device? Establish the relations of h -parameters with these variables for small signal input a.c. signal with a suitable block diagram. Draw the h -parameter a.c. equivalent circuit. $1+3+1=5$
- (e) A negative feedback amplifier has open loop gain -99 . Calculate gain before and after feedback if feedback ratio (β) is 0.05 . State the advantages of negative feedback. $3+2=5$

(4)

GROUP—B

(Marks : 21)

4. Answer any *three* of the following questions :

7×3=21

- (a) Draw the circuit diagram of RC-coupled transistor amplifier. Explain the factors affecting the voltage gain of single-stage RC-coupled amplifier in the low frequency range with its equivalent circuit. Define lower half power frequency. 2+4+1=7
- (b) Draw the circuit diagram of the Wien bridge oscillator and discuss how condition of oscillation is achieved. What is the frequency of oscillation of this type of oscillator? 2+3+2=7
- (c) Explain the operation of an OP-AMP as integrator with a suitable diagram. An OP-AMP is used as integrator with $R = 2 \text{ M}\Omega$ and $C = 0.5 \mu\text{F}$. If input voltage is $0.4t$ volts, calculate output voltage at time $t = 10$ sec. 4+3=7

(5)

(d) State De Morgan's theorem. State why NAND and NOR gates are called universal gates. Show with logic symbol how will you realize (i) NOT gate, (ii) OR gate and (iii) AND gate using NAND gates. What is bubbled AND gate?

2+1+3+1=7

(e) What is SSB transmission? Describe with a block diagram a method of generating single sideband. Show that the maximum power in SSB wave is 25% of unmodulated carrier power when modulation index $m = 1$.

1+4+2=7

(f) Draw the circuit diagram of a Master-Slave JK flip-flop. Explain how race-around condition is avoided by it. Draw the logic symbolic diagram to convert JK flip-flop into D and T flip-flop.

2+3+1+1=7

★ ★ ★